
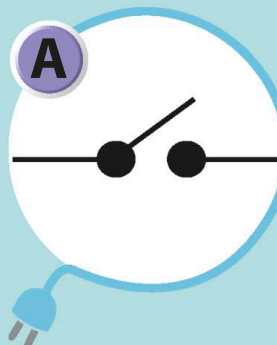




Circuit diagrams

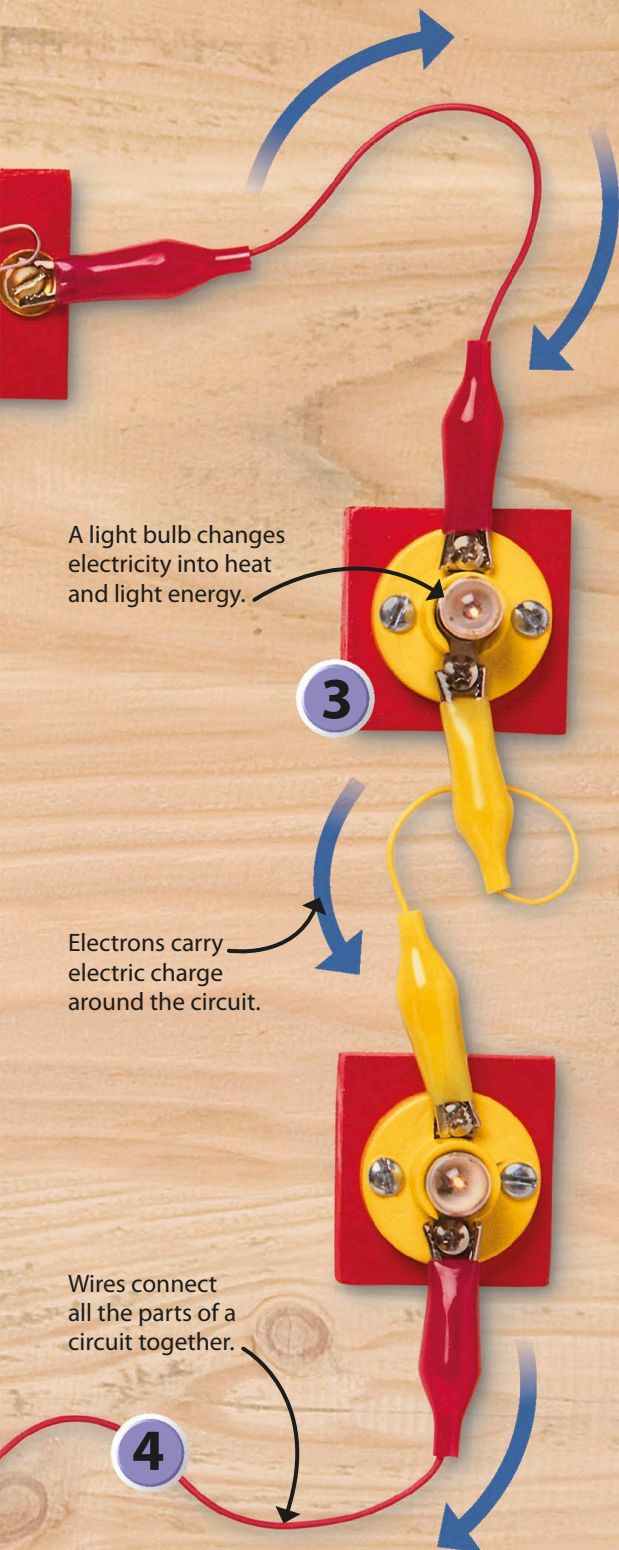If you want to draw a circuit, you don't have to spend time sketching each bit. Instead, you can use special symbols that represent each part. Can you guess which parts match the symbols below?



This part allows the circuit to be broken so the electricity can be turned on or off.

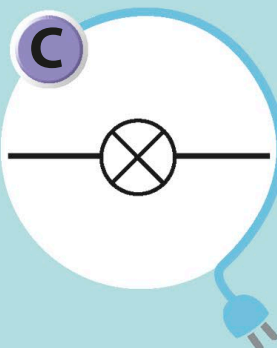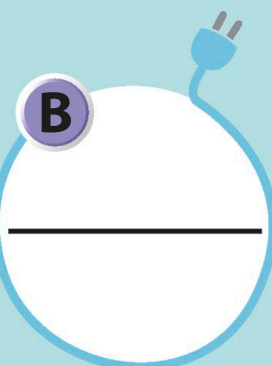These parts are drawn as straight lines connecting the other parts together.



A circle with a cross inside it is used to represent this part, which produces light.

This part powers the circuit and has a positive and negative end.

